

PROJECT 1: ECE 6140

For the four circuits:

s27.chat

s298f_2.chat

s344f_2.chat

s349f_2.chat

You are to develop a circuit simulator and test it with the following inputs for each circuit:

s27.chat

1110101

0001010

1010101

0110111

1010001

s298f_2.chat

10101010101010101

01011110000000111

11111000001111000

11100001110001100

01111011110000000

s344f_2.chat

10101010101010101111111

010111100000001110000000

11111000001111000111111

111000011100011000000000

01111011110000000111111

s349f_2.chat

101010101010101011111111

010111100000001110000000

111110000011110001111111

111000011100011000000000

011110111100000001111111

Your report is to contain:

1. A one-page description of the data structures you used to implement your simulator (max)
2. A one-page description of your simulation algorithm in flow diagram form or pseudo-code.
3. For each circuit simulated, the inputs and outputs in vector form entered into a table (neatly)

Total size of report: 2 pages + simulation data above

Due date: Wednesday October 1st (all students, including video students)